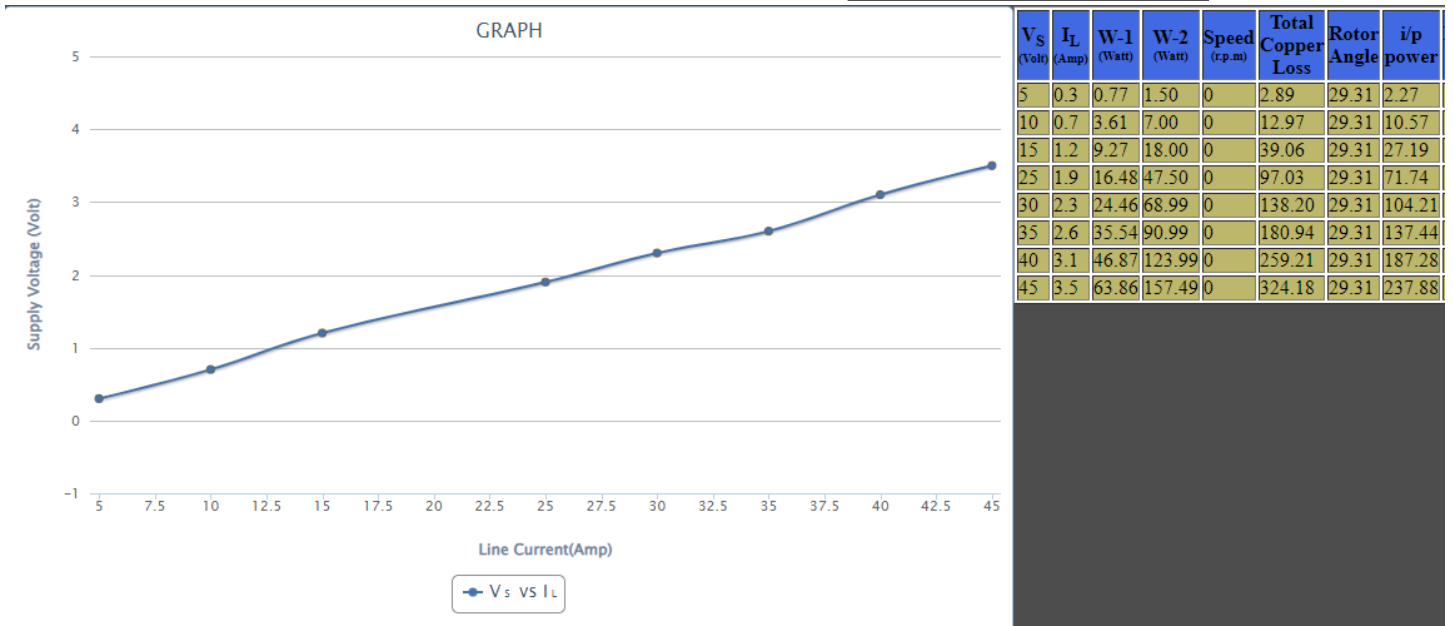
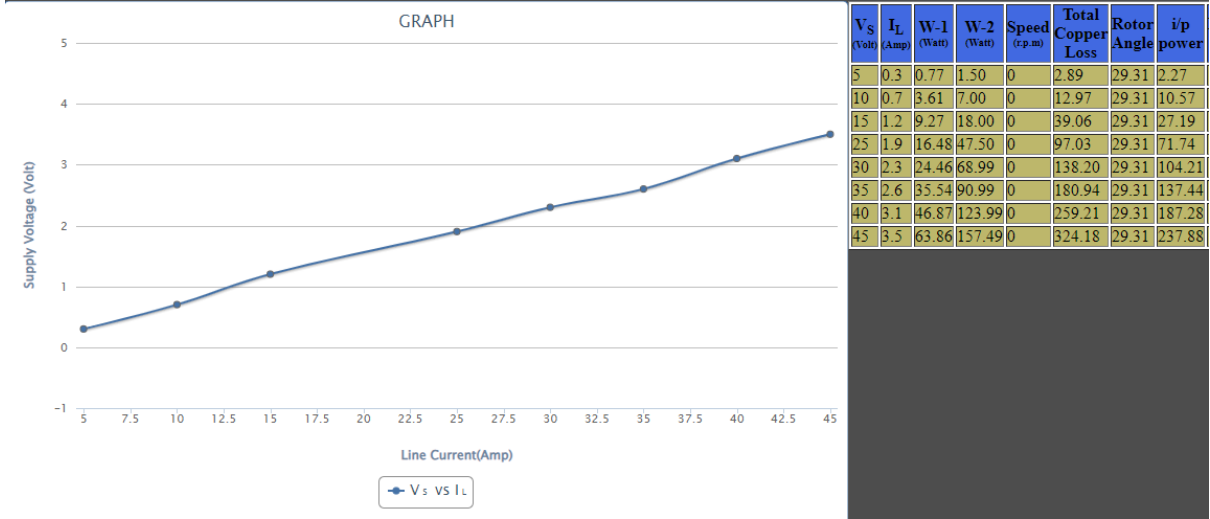
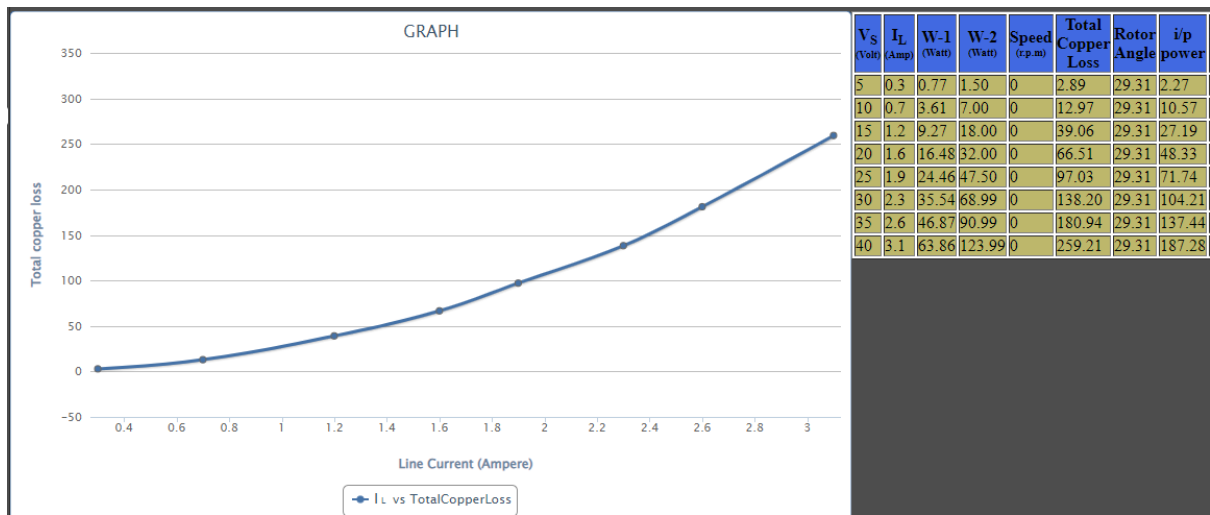
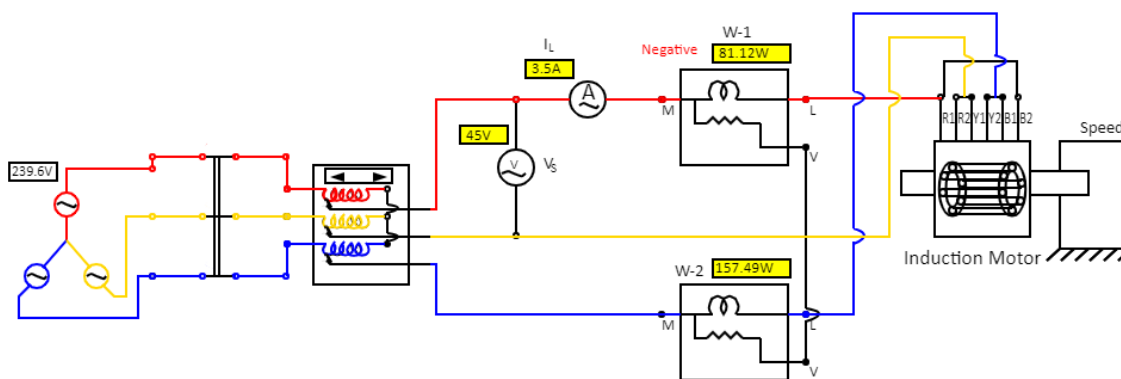






Circuit Diagram: Blocked Rotor Test of Induction Motor



Induction Motor Ratings :

Ratings = 2.2 kW
 Voltage = 415V
 Frequency = 50 Hz
 Speed = 1435 r.p.m.
 p.f. = 0.85
 Winding - Delta

Abbrivations :

V_s = Supply Voltage
 I_L = Line Voltage
 W-1 = First Watt-line ready
 W-2 = Second Watt-line ready