

Experiment-1

V-I Characteristics of a Diode

Site link - vlabs.iitkgp.ernet.in/ke/exp5/index.html#

Aim - To study V-I characteristics of a diode

Apparatus - Forward bias diode [1N4007], resistor, ammeter, etc

Theory - Structure of a P-N junction diode

The diode is a device formed from a junction of n and p-type semiconductor material. Load connected to p-type is anode and to n-type is cathode.

In forward bias, diode +ve terminal of battery is connected to p side and -ve to n side. The holes in p-type and e^- in n-type are pushed towards junction reducing depletion zone width.

In reverse bias, the depletion width increases.

Silicon - In order to conduct forward biasing, voltage should be greater than the barrier potential it acts like closed switch with potential drop of 0.6V across.

In reverse biasing depletion width increases and diode acts like open switch, there is no current flow.

↳ The process is similar for Germanium diode, except that the potential drop is around 0.3V.

Diode Equation

$$I_f = I_s \times \left(\exp \frac{V_f}{n \times V_T} - 1 \right)$$

↓
forward
current





↓
leakage
current

↓
forward
voltage

↓
thermal
voltage

Diagrams →


Structure of P-N Junction Diode

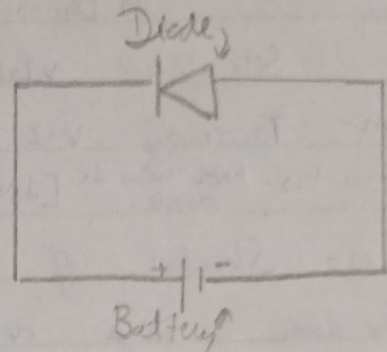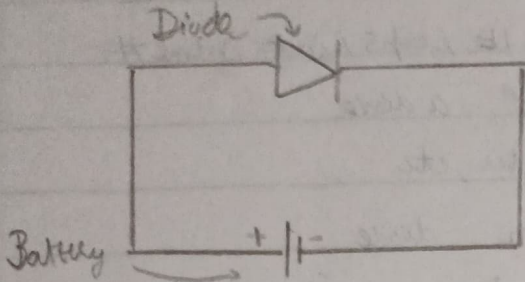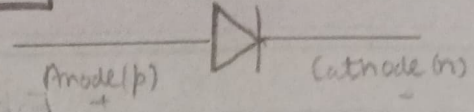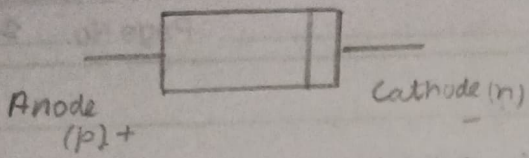

P-N junction diode function in

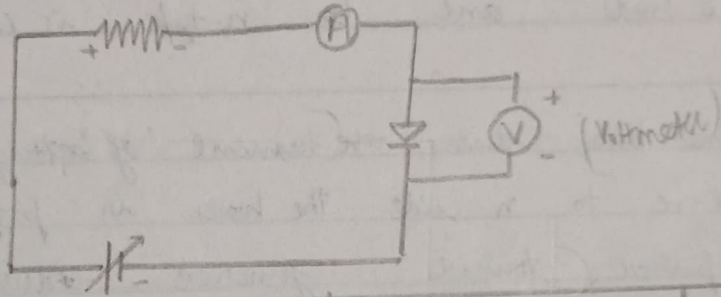(a) fwd bias (Resistor) (Ammeter) (b) reverse bias

[FORWARD BIAS
SILICON DIODE
CKT Diagram
R=100Ω



→ Observation Table

S.No	V _{Battery} (V)	V _R (V)	Forward Voltage (V)	Forward Current (mAmp)	I _x R
1	0.6	0.6	0	0	0
2	0.7	0.172	0.528	0.0958	90.58
3	0.8	0.268	0.532	0.192	19.2
4	0.9	0.365	0.535	0.287	28.7
5	1	0.462	0.538	0.383	38.3
6	1.1	0.56	0.540	0.479	47.9
7	1.4	0.854	0.546	0.766	76.6
8	1.7	1.144	0.551	1.05	105
9	2.3	1.741	0.559	1.63	163
10	2.8	2.236	0.564	2.11	211

Precautions-

1. Proper connection of the circuit (correct polarity, Tight connections)
2. Gradual variation of voltage, limiting current
3. Handling orientation of diode and avoiding overheating

Result/Conclusion-

1. When the forward bias voltage exceeds around $0.6V$ (cut-off voltage)
2. Current increases suddenly, when $V_R = 2.5V$ known as reverse breakdown.

$R = 100 \Omega$

(FORWARD BIAS SILICON DIODE)

S.No	$V_{Battery}$	V_R	Reverse Voltage (V)	Reverse Current (mA)	$V_R = I \times R$
1	0.2	0.3	0.170	0.1	10
2	1.3	0.12	1.18	0.1	10
3	3.7	0.22	3.48	0.1	10
4	5.7	0.26	5.44	0.1	10
5	6.95	0.28	6.6	0.1	10
6	9.15	0.29	8.86	0.1	10
7	11.7	0.30	11.4	0.1	10
8	14.3	0.20	14.1	0.1	10
9	17.95	0.15	17.8	0.1	10
10	20.3	0.10	20.2	0.1	10

$V_R \rightarrow$ Voltage across resistor
 $\Rightarrow (V_B - V_D)$

$R = 1000 \Omega$

FORWARD BIAS

S.No	V_B (V)	V_D (V)	I_D (mA)	$V_R (V_B - V_D)$ (V)	$V_R (I \cdot R)$ (V)
1	0.2	0	0	0.2	0
2	0.7	0.636	0.1	0.17	0.1
3	1	0.539	0.4	0.461	0.4
4	1.3	0.546	0.7	0.714	0.7
5	1.6	0.651	1	1.049	1
6	1.9	0.555	1.3	1.345	1.3
7	2.2	0.588	1.6	1.641	1.6
8	2.5	0.568	1.9	1.937	1.9
9	2.8	0.568	2.2	2.234	2.2
10	3.1	0.571	2.8	3.129	2.8


$V_B \rightarrow$ Voltage of Battery
 $V_D \rightarrow$ Voltage of Diode
 $I_D \rightarrow$ Current of Diode
 $V_R \rightarrow$ Voltage of resistor

SCALE
 1 cm = 0.5 mA (Y-axis)
 2 cm = 0.1 V (X-axis)
 R = 100 Ω


FORWARD BIAS

SCALE
 2 cm = 1 mA (Y-axis)
 1 cm = 0.1 V (X-axis)

R = 2 kΩ

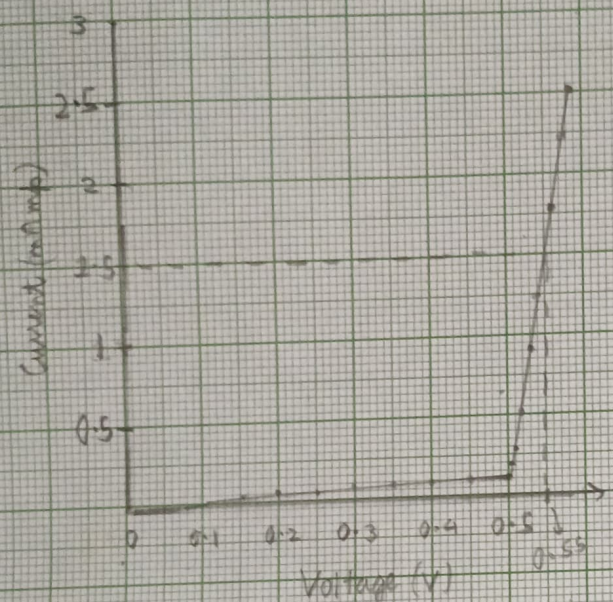


Dynamic resistance → 2.72

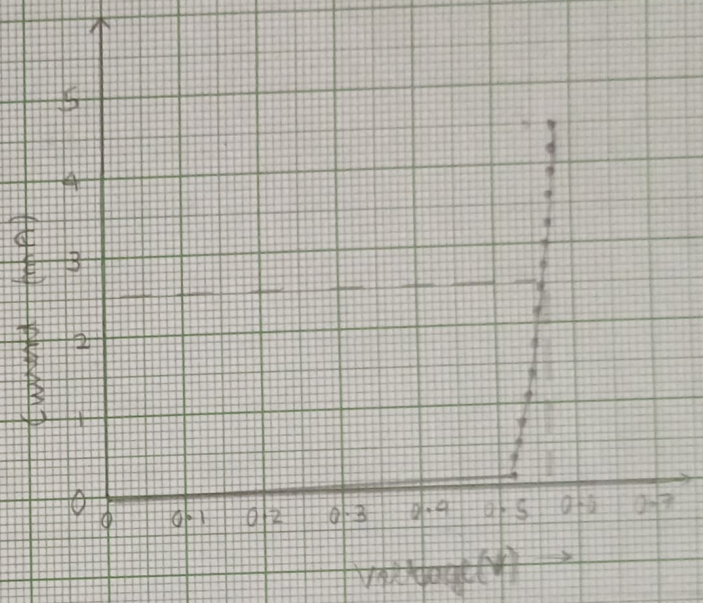

REVERSE BIAS

R = 100 Ω

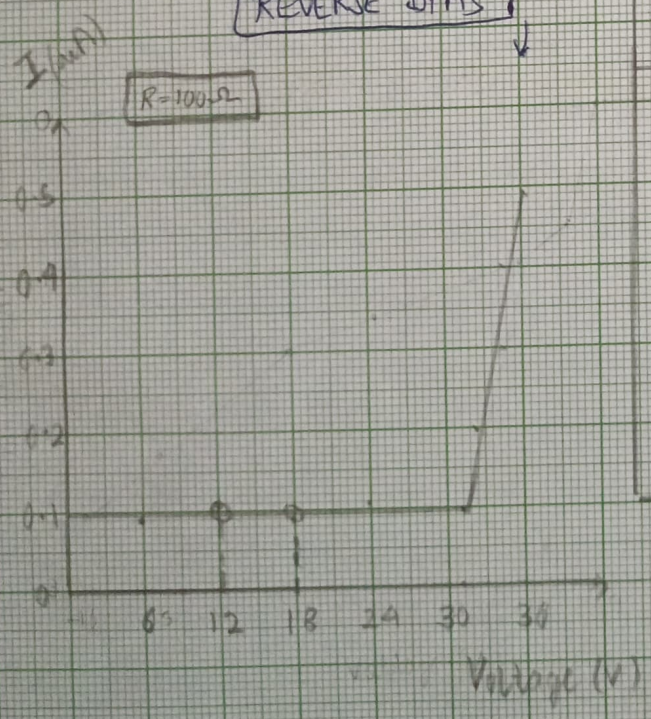

Dynamic resistance

$$\frac{V_2 - V_1}{I_2 - I_1} = \frac{0.5 - 0.0}{0.5 - 0.3} = 0.75$$

→ 0.7509

→ 12.3609

Dynamic Resistance

SCALE
 ① 1 cm = 0.1 mA (Y-axis)
 ② 1 cm = 6 V (X-axis)

$$\frac{0.1 - 0.1}{15 - 2} \rightarrow 0$$