

### Experiment-3

#### Full wave Rectification

Aim- To study full wave rectification

Apparatus- Oscilloscope, resistor ( $R_L$ ), connecting wires

Theory-

Rectification - Device that converts AC to DC. It's of 2 types - a half wave and a full wave rectifier




#### ① Full wave Rectifier

It's exactly the same as half-wave but allows unidirectional current through the load during entire sinusoidal cycle. It converts the whole of the input waveform to one of constant polarity (positive or negative) at its input




#### ② Centre Tapped Transformer

A full wave rectifier can be constructed using centre Tapped transformer. Gives us two shifted sinusoids so exactly one of the waveform is positive at one time. Allows for conduction through load.

→ Diagrams

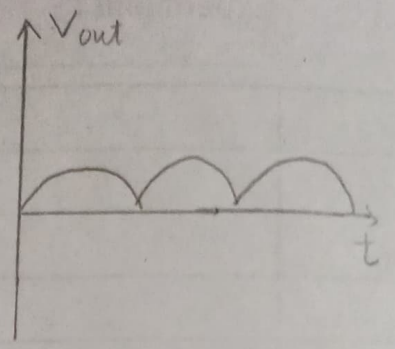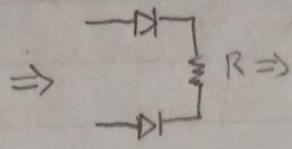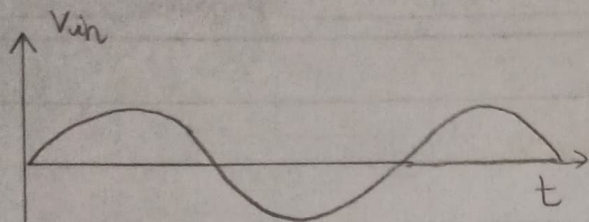


(Full Wave Rectifier)

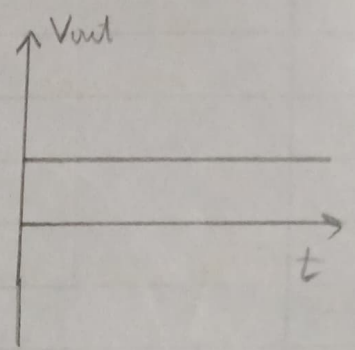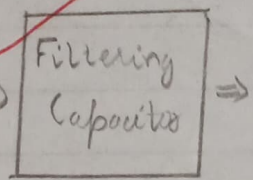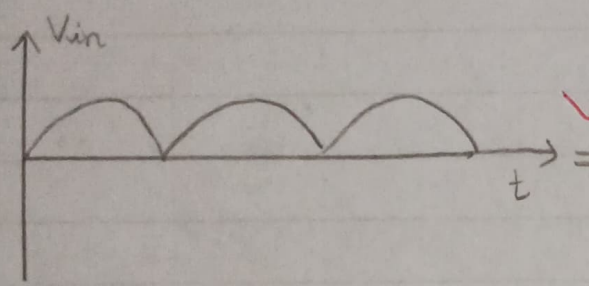

(Capacitive Rectification)

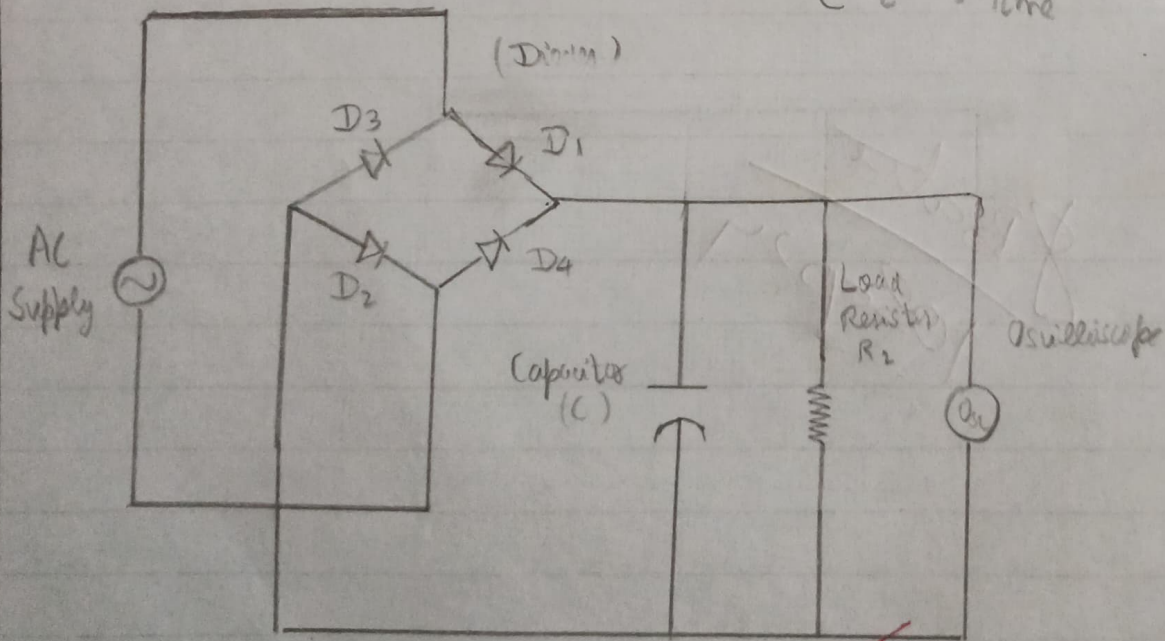$V_{in} \rightarrow V_{in\text{put}}$  (Input Voltage)  
 $V_{out} \rightarrow V_{out\text{put}}$  (Output Voltage)  
 $t \rightarrow$  Time



Ckt diagram for full wave rectifier with filtering

### (B) Bridge Rectifier

It uses 4 rectifying diodes connected in a bridge config. to produce desired output that doesn't require special tapped transformer thereby reducing cost and size.

$$\text{Avg. DC Load Voltage} = V_{oc} = \frac{2V_m}{\pi}$$

$$\text{Avg. Load Current} = \frac{2 \times I_m}{R}$$

$$\text{RMS Load Current} = \frac{I_m}{\sqrt{2}} \quad \text{RMS Load Voltage} = \frac{V_m}{\sqrt{2}}$$

$$\text{Form factor} = \frac{\pi}{2\sqrt{2}} = 1.11 \rightarrow \frac{V_m/\sqrt{2}}{2V_m/\pi}$$

### (2) Capacitive Rectification

↳ Capacitive Rectification - A full wave rectifier converts the whole of input waveform to one of constant polarity at its output. But what is really desired to convert pulsating output of rectifier to a constant DC supply, thus filter input signal.

↳ The simplest kind of filter that can perform filtering task is a capacitor. When connected, the AC components will have a low impedance path to ground and not appear in output.

→ Observation Table

Amp → Amplitude (mV)

1. Full Wave Rectifier

(a) Set 1

freq = 1000Hz

$R_L = 500\Omega$

(b) Set 2

freq = 1000Hz

$R_L = 400\Omega$

(c) Set 3

freq = 1000Hz

$R_L = 300\Omega$

(A)

S.No	Amp (V)	Peak Current (mA)
1	0	-1.4
2	0.5	-0.400
3	1	0.799
4	1.5	1.599
5	2	2.59

(B)

S.No	Amp (V)	Peak Current (mA)
1	0	-1.74
2	0.5	0.71
3	1	0.74
4	1.5	1.749
5	2	2.749

(C)

S.No	Amp (V)	Peak Current (mA)
1	0	-2.33
2	0.5	-0.66
3	1	0.91
4	1.5	2.33
5	2	4.33

## Ripple Voltage and Ripple Factor

A new charging pulse occurs every half cycle the capacitor charges and discharges very quickly

The variable portion is known as ripple

Further, ratio of ripple voltage to avg. voltage is ripple factor.

### ↳ Precaution

- 1) Check the capacitor polarity
- 2) Monitor ripple voltage across load.
- 3) Ensure proper oscilloscope probing
- 4) Check diode orientation and connection

### ↳ Conclusion

↳ In this experiment, using a bridge rectifier with 4 diodes, both halves of AC waveform into pulsating DC output. Bridge rectifier provides a more efficient rectification process by utilizing entire AC cycle. The inclusion of capacitor reduced ripple in rectified output resulting in a constant DC voltage.

*J. B. D.*

23/9/29

## ② Capacitive Rectification

$$V_{p_{in}} = 1V$$

Position Y-axis = 0.1

Phase = 0 deg

Freq = 1000 Hz

$$V_{p_{out}} = 1V$$

Position X-axis = 0.1

Phase = 0 deg

freq = 1000 Hz


Oscilloscope Least Count = 0.01 (for Voltage)  
1 ms (for time)

→ Calculations

$$\text{Form factor} = \frac{V_{rms}}{V_{avg}} \Rightarrow \frac{V_m/\sqrt{2}}{2V_m/\pi} \Rightarrow \frac{\pi}{2\sqrt{2}} = 1.11$$

$$\text{Ripple Factor} \Rightarrow \gamma \Rightarrow \sqrt{(\text{Form factor})^2 - 1} \times 100\% \\ \hookrightarrow 48.1\%$$

### (a) Full Wave Rectifier

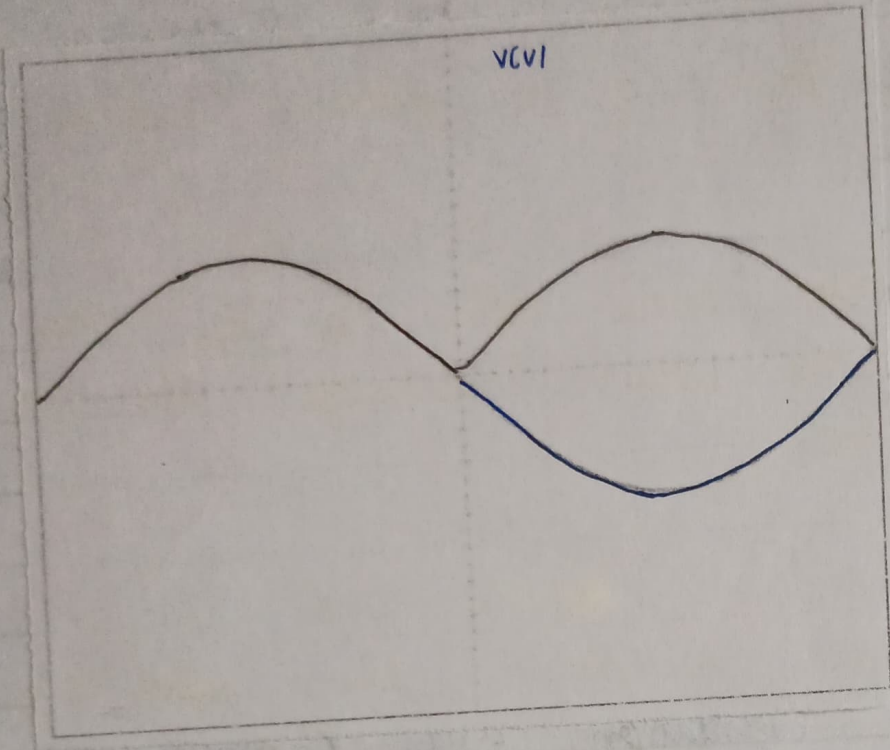

Black line represents rectified output DC and blue line represents input AC


frequency = 1000 Hz

Amplitude = 1 V

$R_L = 500 \Omega$

(Load resistance)

### (b) Capacitive Rectification

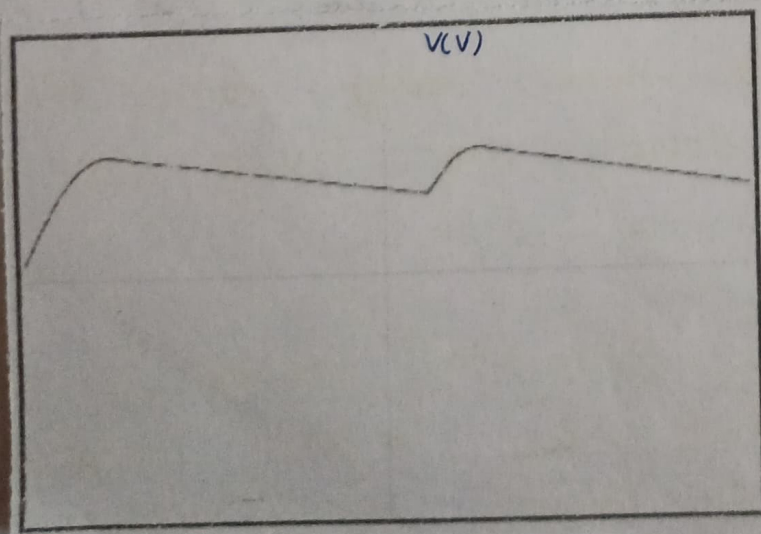

Rectified Output DC

frequency = 1000 Hz