

Experiment-8

Differentiator and Integrator using Op-Amp

Aim - To study Differentiator and integrator using op-amp.

Apparatus - Op-amp, connecting wires, resistors, oscilloscope, capacitor

Theory

Op amp is a linear electronic device having three terminals, 2 high impedance input and one output terminal. Op-amp can perform multiple function when attached to different feedback combinations. Generally, used as one voltage amplifier.


1) The Integrator

Its a circuit designed with op-amp so that it performs mathematical integration operation. Its output is proportional to amplitude and time duration of input. Feedback resistor replaced by capacitor. The results in ratio of capacitor impedance and input resistance increasing, causing a linearly increasing amp output voltage that continues to increase until capacitor becomes fully charged.


$$V_c = \frac{Q}{C} \quad I_{in} = \frac{V_{in} - 0}{R_{in}}$$

* DIAGRAM

(1) The Integrator

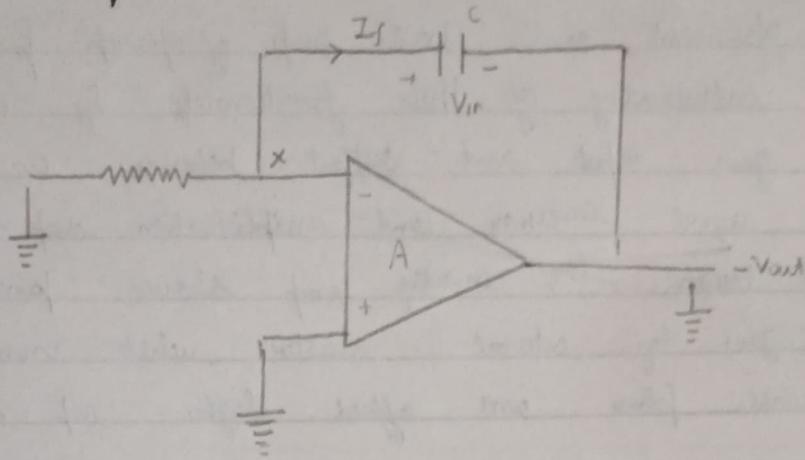

(2) The differentiator

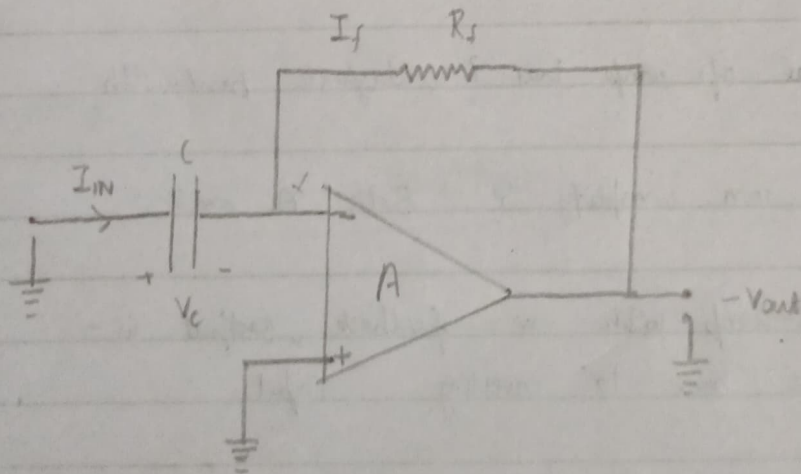

$$I_f = C \times \frac{dV_{out}}{dt} = C \times \frac{1}{C} \times \frac{dQ}{dt} = \frac{dQ}{dt}$$

$$\text{So, } V_{out} = \frac{-1}{R_{in} \times C} \int V_{in} dt$$

$$V_{out} = \frac{-1}{j \times \omega R_{in} \times C} \times V_{in}$$

2) The differentiator

In differentiation circuit, input is connected to inverting output of op-amp through C and negative feedback is applied to inverting input through R_f . Circuit provides mathematical differentiation operation and output is first derivative of input signal.

$$I_{in} = I_f = \frac{-V_{out}}{R_f}$$

$$I_f = C \times \frac{dV_{in}}{dt} = I_{in}$$

$$\frac{-V_{out}}{R_f} = C \times \frac{dV_{in}}{dt}$$

$$V_{out} = -R_f \times C \times \frac{dV_{in}}{dt}$$


* Precaution :-

- 1) Verify the power supply voltage matches op-amp.
- 2) Ensure proper grounding to prevent noise.
- 3) Avoid overheating by proper ventilation.

* GRAPH


Light blue - Input waveform
Blue - Output waveform

① Integrator

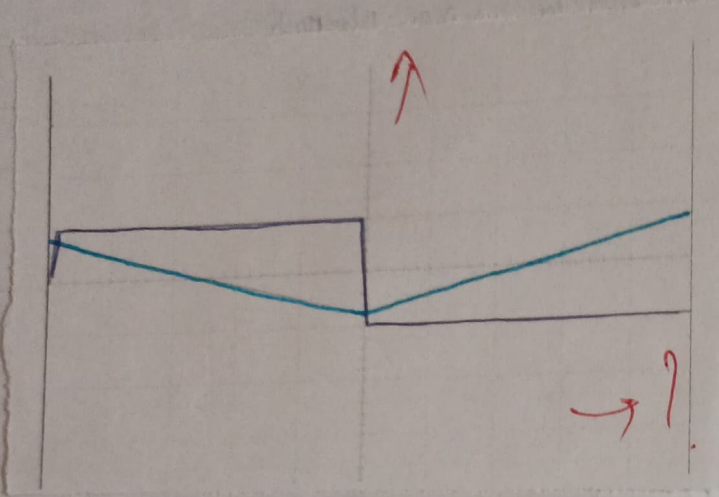

(a) Square wave
freq = 3000 Hz
Amplitude = 0.5 V

(b) Sine wave

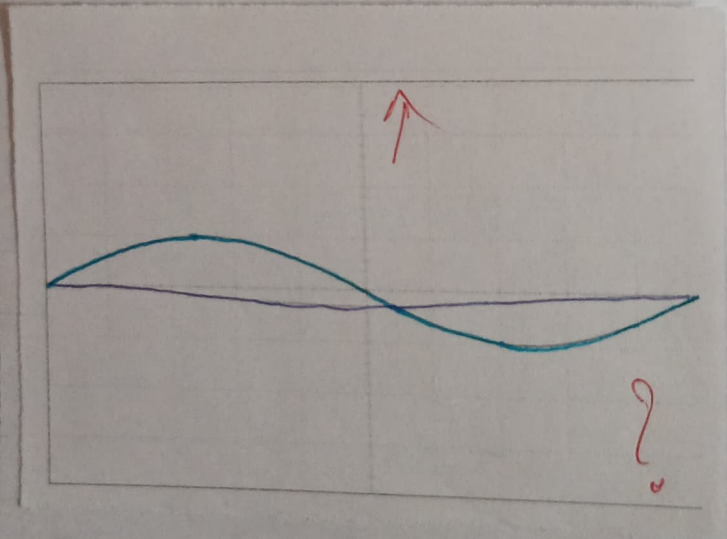

freq = 3000 Hz
Amplitude = 0.5 V

Experiment :

Date _____

Page No. _____

Conclusion


The experiment on differentiator and integrator circuits using op-amp demonstrated their functionality in signal processing. The differentiator does mathematical differentiation and integrator does mathematical integration.

The practical implementation validated the theoretical concepts by observing expected phase shifts and waveform

GRAPHS

② Differentiators

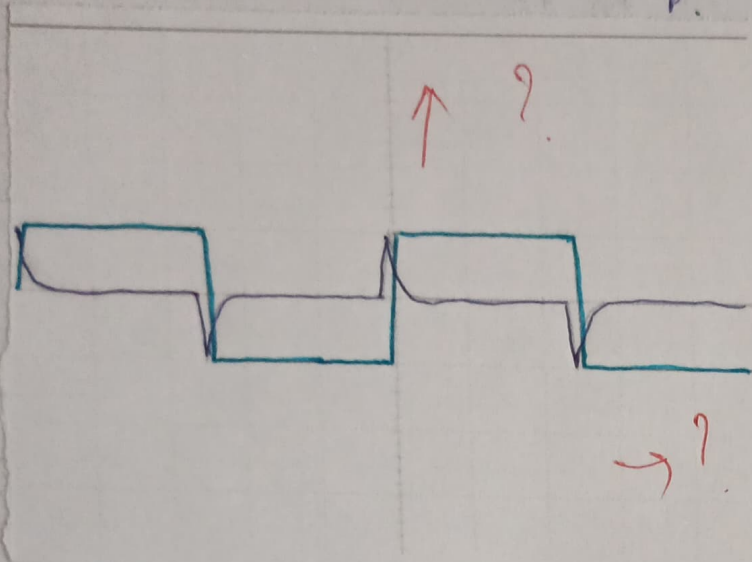a) Square wave \rightarrow freq. = 2000Hz
Amp. = 1V



(b) Sine wave freq. = 2000Hz
Amp. = 1V

